Course project

Modified DP

Instruction set

- rrr register
- Aaaaaa –MA
- iiiiiiii imm.

Instruction	Encoding	Operation	Comment

Data movement instructions

LDA A,rrr	0001 0rrr	$A \leftarrow R[rrr]$	Load accumulator from register
STA rrr,A	0010 0rrr	$R[rrr] \leftarrow A$	Load register from accumulator
LDM A,aaaaaa	0011 0000	$A \leftarrow M[aaaaaa]$	Load accumulator from memory
	00aaaaaa		
STM aaaaaa,A	0100 0000	M[aaaaaa] ← A	Load memory from accumulator
	00 aaaaaa		
LDI A,iiiiiiii	0101 0000	A ← iiiiiiii	Load accumulator with immediate
	iiiiiiii		value (iiiiiiii is a signed number)

Arithmetic and logical instructions

AND A,rrr	1010 Orrr	$A \leftarrow A \text{ AND R[rrr]}$	Accumulator AND register
OR A,rrr	1011 Orrr	$A \leftarrow A \text{ OR R[rrr]}$	Accumulator OR register

ADD A,rrr	1100 Orrr	$A \leftarrow A + R[rrr]$	Accumulator + register
SUB A,rrr	1101 Orrr	$A \leftarrow A - R[rrr]$	Accumulator – register
NOT A	1110 0000	$A \leftarrow NOT A$	Invert accumulator
INC A	1110 0001	$A \leftarrow A + 1$	Increment accumulator
DEC A	1110 0010	$A \leftarrow A - 1$	Decrement accumulator
SHFL A	1110 0011	A ← A << 1	Shift accumulator left
SHFR A	1110 0100	$A \leftarrow A >> 1$	Shift accumulator right
ROTR A	1110 0101	$A \leftarrow Rotate_right(A)$	Rotate accumulator right

Instruction set

Jump instructions

• Smmm –Sign and magn.

is .		+
0110 0000	PC = aaaaaa	Absolute unconditional jump
00 aaaaaa		
0110 smmm	if (smmm != 0) then	Relative unconditional jump (smmm
	if $(s == 0)$ then $PC = PC + mmm$	is in sign and magnitude format)
	else $PC = PC - mmm$	
0111 0000	if (A == 0) then PC = aaaaaa	Absolute jump if A is zero
00 aaaaaa		
0111 smmm	if $(A == 0 \text{ and smmm } != 0)$ then	Relative jump if A is zero (smmm is
	if $(s == 0)$ then $PC = PC + mmm$	in sign and magnitude format)
	else $PC = PC - mmm$	
1000 0000	if (A!=0) then PC = aaaaaa	Absolute jump if A is not zero
00 aaaaaa		
1000 smmm	if (A != 0 and smmm != 0) then	Relative jump if A is not zero
	if $(s == 0)$ then $PC = PC + mmm$	(smmm is in sign and magnitude
	else $PC = PC - mmm$	format)
1001 0000	if(A == positive) then PC = aaaaaa	Absolute jump if A is positive
00 aaaaaa		
1001 smmm	if(A == positive and smmm!= 0) then	Relative jump if A is positive (smmm
	if $(s == 0)$ then $PC = PC + mmm$	is in sign and magnitude format)
	else $PC = PC - mmm$	
	0110 0000 00 aaaaaa 0110 smmm 0111 0000 00 aaaaaa 0111 smmm 1000 0000 00 aaaaaa 1000 smmm	0110 0000 PC = aaaaaa 01 10 smmm if (smmm != 0) then if (s == 0) then PC = PC + mmm if (A == 0) then PC = aaaaaa 0111 0000 if (A == 0) then PC = aaaaaa 0111 smmm if (A == 0 and smmm != 0) then if (s == 0) then PC = PC + mmm if (A != 0) then PC = aaaaaa 1000 0000 if (A != 0 and smmm != 0) then if (s == 0) then PC = PC + mmm if (A == positive) then PC = aaaaaa 1001 0000 if (A == positive) then PC = aaaaaa 1001 smmm if (A == positive and smmm != 0) then if (s == 0) then PC = PC + mmm

Input / Output and Miscellaneous


In A	1111 0000	$A \leftarrow input$	Input to accumulator
Out A	1111 0001	$output \leftarrow A$	Output from accumulator
HALT	1111 0010	Halt	Halt execution
NOP	0000 0000	no operation	No operation


Modified DP

Added

to the


cycle

 

 


Fetch in Cycle 0

 - IR loaded in Cycle 0 with the first byte (could be the only byte) of Instruction.
- It is provided to CU in the beginning of the Cycle 1, the decode delay is included into the cycle (as in multi-cycle MIPS) and the decision is made on the control signals to assert in the second cycle: Cycle 1
- PC is incremented and loaded.



 
LDM A,aaaaaa $\begin{bmatrix} 0011\ 0000 & A \leftarrow M[aaaaaa] \\ 00aaaaaaa & \end{bmatrix}$




LDM Cycle 2: reads the IR. The byte is the memory addre and it is given to Memory for reading data into Accumulator:

storing Accumulator. Done Load 8-bit Register
Clear IR
IR₁₋₀ IRload_dp imm_dp IR_dp_{7-0} MRload rěl LoadClear MA Pmux_dp D₅₋₀ Load 6-bit Register Cload_dp -8 1c_amuxout Clear A coumulator Q_{7-0} MemInst_dp → 64 locations x 8 bits $+^3_{IR_{2-0}}$ RAM Address_{s-0} MemWr_dp → the timing former cory access. Asel_dp₂₋₀ → A load_dp → WE 8 Register File clock. c_rfout Aeq0_dp -Apos_dp ◀ RFwr_dp → ALU $\texttt{ALUsel_dp}_{2,1,0} \bullet$ _c_aluout sel_{i,0} Shifter $\verb|Shiftsel_dp|_{1,0}$ _c_shiftout outen_dp → OutputReg output_dp

 STM Cycle 2: reads Memory address is given to Memory f storing Accumulator. Done




 
Register ALU op Cycle 1: perform the operation; increment PC





Read 6 bits ofthe 2 nd byte to PC

 

 

Cycles per instruction

- Some instructions complete in 2 cycles , such as NOP and Halt (Fetch and Decode), jumps, arithmetic, in, out
- LDM and STM complete in 3 cycles
- Unfinished FSM is shown

